



Full resolution photo on my Instagram [@feenafoto](#)



@feenafoto

1

ECOR1043: Circuits


Multi-Node Analysis

Develop systematic techniques to determine all the voltages in a circuit

3

Nodal Analysis

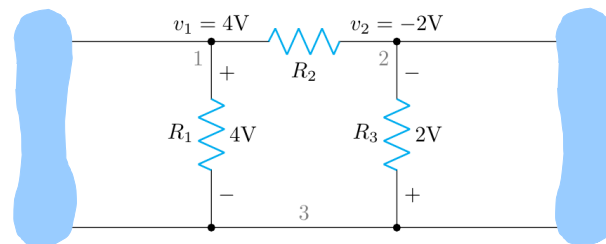- A Multi-Node circuit is a circuit with more nodes than the basic node pair circuit we discussed
 - Due to the added nodes, analysis becomes more complex
 - Therefore, we introduce a new type of analysis
- Multi-Node Analysis: Nodal Analysis
 - This method uses the “Nodal” equations of [Kirchhoff's Current Law](#) as well as [Ohm's Law](#) to find the [voltages](#) around the circuit.




4

4

Nodal Analysis

- Before we start: Set a reference node (ground)
 - [Defining the reference node is vital](#): The statement $V_1=4V$ is [meaningless](#) by itself without a reference
 - Therefore, to give the measurement meaning [we assume the reference is ground](#)
 - Any node voltage (i.e., v_1 , and v_2) is measured in reference to ground [unless otherwise defined](#) (e.g., voltage difference between two points)

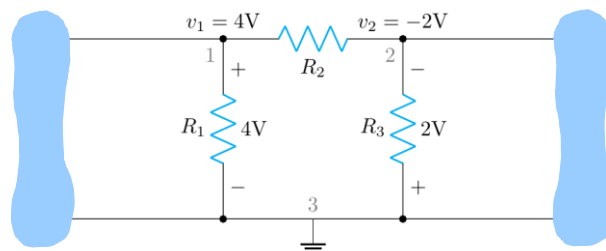


What if we want to solve for $v_{12} = ____?$ or $v_{21} = ____?$

5

5

Nodal Analysis

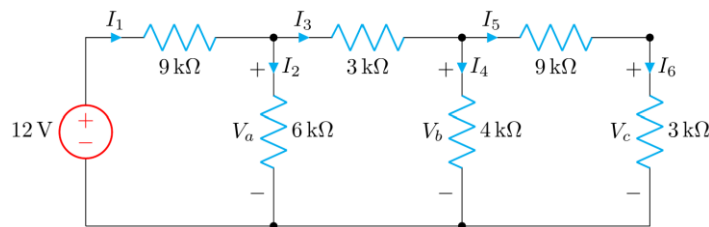- Steps for Nodal Analysis:
 - 1) Identify all nodes and select a **reference node**
 - 2) Identify all **known** node voltages
 - 3) At each node with an unknown voltage, write a **KCL equation**
 - 4) Replace currents in terms of node voltages
 - 5) Solve for unknown voltages as needed
 - 6) Use voltages to solve for any desired values




6

6

Nodal Analysis

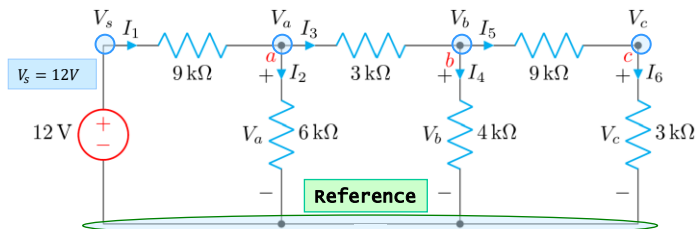- Ex. 1: Find the equations to determine the unknown node voltages



$$\text{@ node a: } \sum_{k=1}^n i_k = 0$$

$$-I_1 + I_2 + I_3 = 0$$

$$\text{@ node b: } \sum_{k=1}^n i_k = 0$$

$$-I_3 + I_4 + I_5 = 0$$

$$\text{@ node c: } \sum_{k=1}^n i_k = 0$$

$$-I_5 + I_6 = 0$$

Steps:

1) Identify all nodes and select a reference node

2) Identify all known node voltages


3) At each node with an unknown voltage, write a KCL equation (For this example, assume currents entering the nodes are negative)

7

7

Nodal Analysis

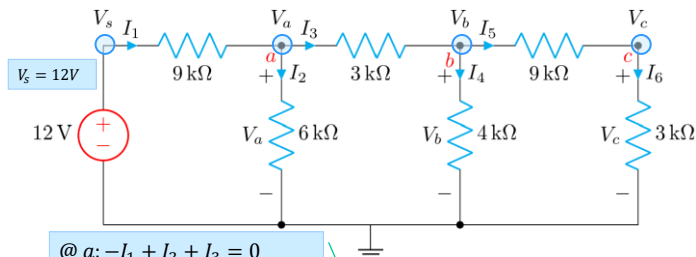- Ex. 1: Find the equations to determine the unknown node voltages



$$\text{@ } a: -I_1 + I_2 + I_3 = 0$$

$$-\frac{V_s - V_a}{9k} + \frac{V_a}{6k} + \frac{V_a - V_b}{3k} = 0$$

$$\text{@ } b: -I_3 + I_4 + I_5 = 0$$

$$-\frac{V_a - V_b}{3k} + \frac{V_b}{4k} + \frac{V_b - V_c}{9k} = 0$$

$$\text{@ } c: -I_5 + I_6 = 0$$

$$-\frac{V_b - V_c}{9k} + \frac{V_c}{3k} = 0$$

Shortcut: Skip writing these equations...

Practice writing these directly

These are the three equations to solve for three unknowns V_a, V_b, V_c

Steps:

- 1) Identify all nodes and select a reference node
- 2) Identify all known node voltages
- 3) At each node with an unknown voltage, write a KCL equation (For this example, assume currents entering the nodes are negative)
- 4) Replace currents in terms of node voltages ($I=V/R$)

8

8

Nodal Analysis

- Ex. 2: Find the equations to determine unknown voltages V_1 and V_2

Steps:

- 1) Identify all nodes and select a reference node
- 2) Identify all known node voltages
- 3) Write a KCL equation for rest of the nodes

@ Node 1: Sum of currents=0

Assuming:

- All the currents are **leaving** the node
- Currents **leaving** the node are **positive**


$$I_a + I_b + I_c + I_d = 0$$

Note: $I_a = i_1$

$$i_1 + I_b + I_c + I_d = 0$$

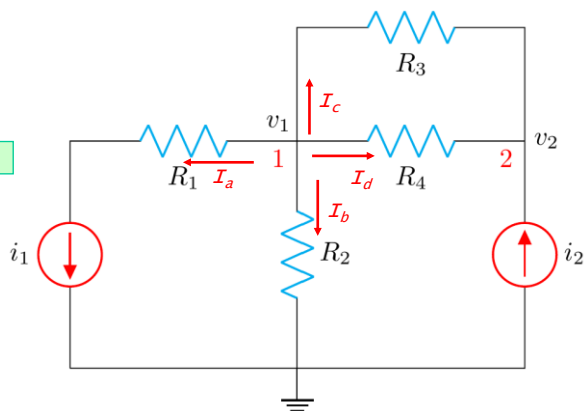4) Replace currents in terms of node voltages

$$i_1 + \frac{v_1}{R_2} + \frac{v_1 - v_2}{R_3} + \frac{v_1 - v_2}{R_4} = 0$$



9

9

Nodal Analysis

- Ex. 2 (cont.): Find the equations to determine voltages V_1 and V_2

@ Node 2: Sum of currents=0

Assuming:

- All the currents are **entering** the node
- Currents **entering** the node are **positive**

$$I_g + I_e + I_f = 0$$

Note: $I_e = I_c$, $I_f = I_d$, and $I_g = i_2$


4) Replace currents in terms of node voltages

$$i_2 + \frac{v_1 - v_2}{R_3} + \frac{v_1 - v_2}{R_4} = 0$$

Now we have two eq which can be solved for two unknowns (i.e. v_1 & v_2)

$$i_1 + \frac{v_1}{R_2} + \frac{v_1 - v_2}{R_3} + \frac{v_1 - v_2}{R_4} = 0$$
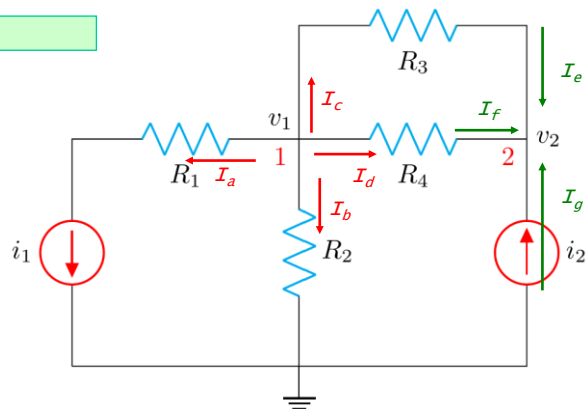
$$i_2 + \frac{v_1 - v_2}{R_3} + \frac{v_1 - v_2}{R_4} = 0$$



10

Nodal Analysis

- Ex. 3: Find all the branch currents.

One node is connected to the reference via a voltage source, so voltage is known at V_1

$$V_1 = -3 \text{ V}$$

Assuming:

- All currents are **leaving** node 2
- Currents **leaving** the nodes are **positive**

Apply KCL at node 2

$$I_1 + I_2 + I_3 = 0$$

$$I_3 = 6 \text{ mA}$$

Replace currents in terms of node voltages and known values and solve for V_2

$$\frac{V_2}{2 \text{ k}\Omega} + \frac{V_2 - V_1}{1 \text{ k}\Omega} + 6 \text{ mA} = 0$$

$$V_1 = -3 \text{ V}$$


$$\frac{V_2}{2 \text{ k}\Omega} + \frac{V_2 - (-3)}{1 \text{ k}\Omega} + 6 \text{ mA} = 0$$

$$\frac{V_2}{2 \text{ k}\Omega} + \frac{V_2 + 3}{1 \text{ k}\Omega} + 6 \text{ mA} = 0$$

$$V_2 + 2V_2 + (2 \times 3) + 12 = 0$$

$$3V_2 + 18 = 0$$

$$V_2 = -6 \text{ V}$$

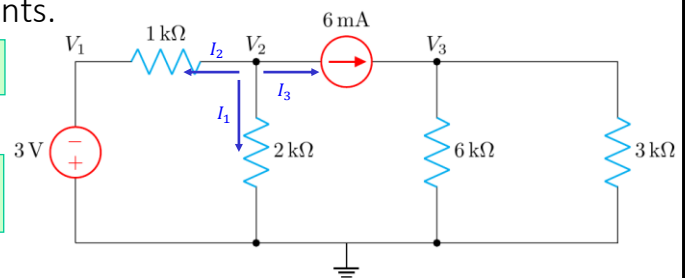

11

Nodal Analysis

- Ex. 3 (cont.): Find all the branch currents

Assuming:

- All currents are **leaving** node 3
- Currents **leaving** the nodes are **positive**

Apply KCL at node 3

$$I_a + I_b + I_c = 0$$

$$I_a = -6 \text{ mA}$$

$$-6 \text{ mA} + I_b + I_c = 0$$


Replace currents in terms of node voltages and known values and solve for V_3

$$-6 \text{ mA} + \frac{V_3}{6 \text{ k}\Omega} + \frac{V_3}{3 \text{ k}\Omega} = 0$$

$$-36 + V_3 + 2V_3 = 0$$

$$3V_3 = 36$$

$$V_3 = \frac{36}{3} = 12 \text{ V}$$

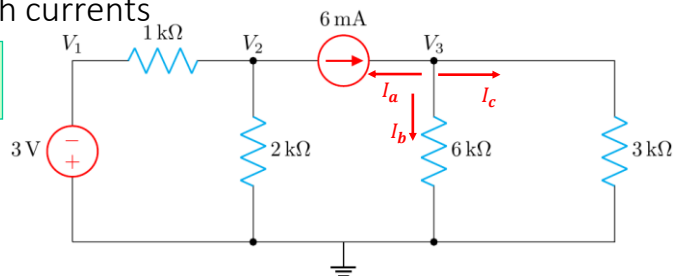

12

12

Nodal Analysis

- Ex. 3 (cont.): Find all the branch currents

We now have:

$$V_1 = -3 \text{ V}$$

$$V_2 = -6 \text{ V}$$

$$V_3 = 12 \text{ V}$$

Use Ohm's Law to find I_1 , I_2 , I_b and I_c :

$$V = IR$$

$$I_1$$


$$I_1 = \frac{V_2}{2 \text{ k}\Omega}$$

$$I_1 = \frac{-6 \text{ V}}{2 \text{ k}\Omega} = -3 \text{ mA}$$

$$I_2$$

$$I_2 = \frac{V_2 - V_1}{1 \text{ k}\Omega}$$
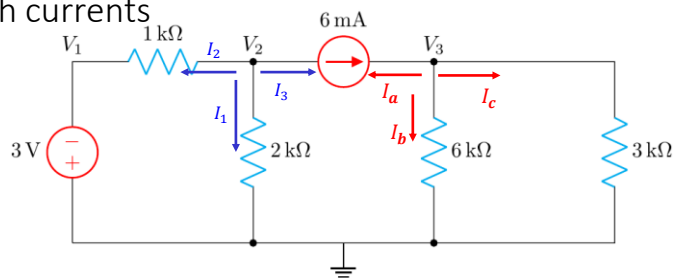
$$I_2 = \frac{-6 - (-3)}{1 \text{ k}\Omega} = -3 \text{ mA}$$



$$I_b$$

$$I_b = \frac{V_3}{6 \text{ k}\Omega}$$

$$I_b = \frac{12 \text{ V}}{6 \text{ k}\Omega} = 2 \text{ mA}$$

$$I_c$$

$$I_c = \frac{V_3}{3 \text{ k}\Omega}$$

$$I_c = \frac{12 \text{ V}}{3 \text{ k}\Omega} = 4 \text{ mA}$$

Do these values make sense?
How can you check?

13

13

Nodal Analysis

- Ex. 3 (cont.): Find all the branch currents

– Alternate solution for I_b and I_c :

To find I_b and I_c apply current divider:

I_b


$$I_b = \frac{3k\Omega}{3k\Omega + 6k\Omega} \times 6mA = 2mA$$

$$I_b = 2mA$$

I_c

$$I_c = \frac{6k\Omega}{6k\Omega + 3k\Omega} (6mA)$$


$$I_c = 4mA$$

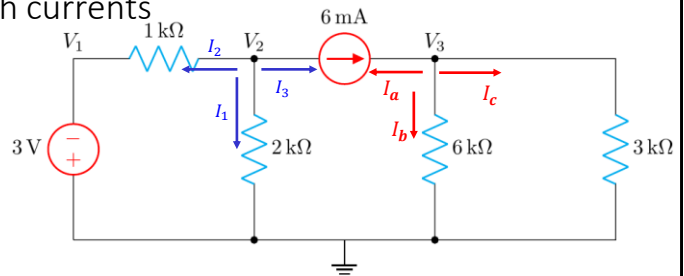

Recall current divider

$$i_1 = \frac{R_2}{R_1 + R_2} \times I$$

$$i_2 = \frac{R_1}{R_1 + R_2} \times I$$

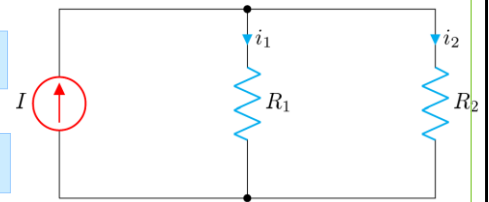

14

14

Multi-node Analysis

- Ex. 4: Solve for V_1 , V_2 , and V_3


3 nodes plus the reference. In principle we need 3 equations.

Two nodes are connected to the reference through voltage sources. Hence, those node voltages are known implicitly.

$$V_1 = 12V$$

$$V_3 = -6V$$

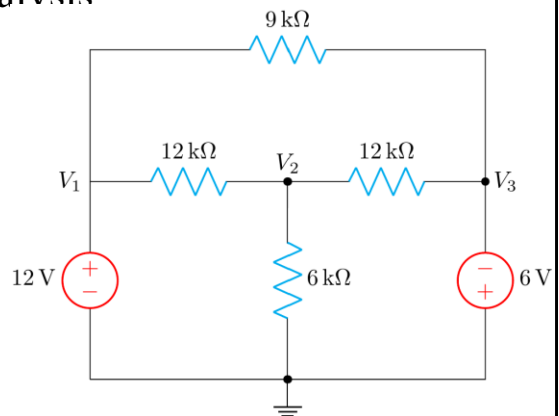Therefore, only one KCL equation is necessary (to V_2)



15

15

Multi-node Analysis

- Ex. 4 (cont.): Solve for V_1 , V_2 , and V_3

$$V_1 = 12 \text{ V}$$

$$V_3 = -6 \text{ V}$$

$$V_2 = ? \text{ V}$$

Assuming all currents are **leaving**,
and currents **leaving** are **positive**

To find V_2 , apply KCL at node V_2

$$I_1 + I_2 + I_3 = 0$$

Replace currents in terms of node voltages

$$\frac{V_2}{6k\Omega} + \frac{V_2 - V_3}{12k\Omega} + \frac{V_2 - V_1}{12k\Omega} = 0$$

Solve for V_2 (the only unknown)

$$\left(\frac{V_2}{6k\Omega} + \frac{V_2 - V_3}{12k\Omega} + \frac{V_2 - V_1}{12k\Omega} \right) \times 12k = 0 \times 12k$$


$$2V_2 + V_2 - V_3 + V_2 - V_1 = 0$$

$$4V_2 - V_3 - V_1 = 0$$

$$4V_2 - (-6) - 12 = 0$$

$$4V_2 + 6 - 12 = 0$$

$$V_2 = \frac{6}{4} = 1.5 \text{ V}$$

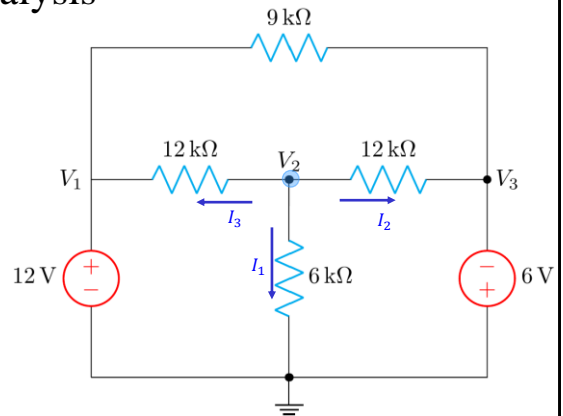

16

16

Practice Problems

17

17

Multi-node Analysis

- Prob. 1: Calculate the node voltages

Apply KCL and Ohm's law at node 1

$$i_1 = i_2 + i_3$$

$$5 = (v_1 - v_2)/4 + (v_1 - 0)/2$$

$$20 = v_1 - v_2 + 2v_1$$

$$3v_1 - v_2 = 20$$

→ A

Apply KCL and Ohm's law at node 2


$$i_2 + i_4 = i_1 + i_5$$

$$(v_1 - v_2)/4 + 10 = 5 + (v_2 - 0)/6$$

$$3v_1 - 3v_2 + 120 = 60 + 2v_2$$

$$3v_1 - 5v_2 = -60$$

→ B

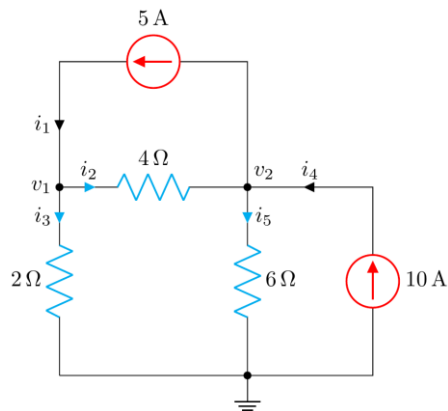

18

18

Multi-node Analysis

- Prob. 1(cont.): Calculate the node voltages

We now have two equations and two unknowns

$$3v_1 - v_2 = 20$$

→ A

$$3v_1 - 5v_2 = -60$$

→ B

Subtract B from A

$$4v_2 = 80$$

$$v_2 = 20V$$

Substitute v_1 back in equation A


$$3v_1 - v_2 = 20$$

→ A

$$3v_1 - 20 = 20$$

$$3v_1 = 40$$

$$v_1 = \frac{40}{3} = 13.33V$$

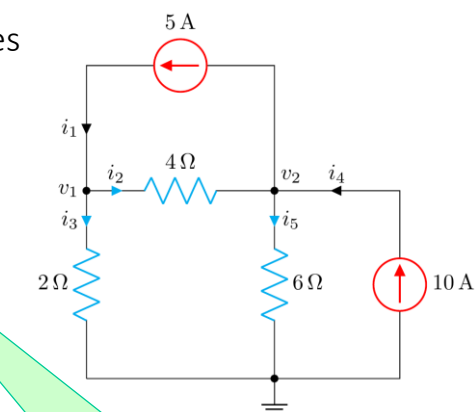

You can use any method that you know to solve the two equations for two unknown voltages. I am using method of elimination

19

19

Multi-node Analysis

- Prob. 2: Given: $i_A = 1mA$, $R_1 = 12k\Omega$, $R_2 = 6k\Omega$, $i_B = 4mA$ and $R_3 = 6k\Omega$. Determine all node voltages and branch currents.

Apply KCL at node 1 (assuming current into the node are $-ve$)

$$-i_A + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} = 0$$

$$-1m + \frac{v_1}{12k} + \frac{v_1}{6k} - \frac{v_2}{6k} = 0$$

$$\frac{v_1}{4k} - \frac{v_2}{6k} = 1 \times 10^{-3}$$

→ A

Apply KCL at node 2 (assuming current into the node are $+ve$)


$$-i_B - \frac{v_2}{R_3} + \frac{v_1 - v_2}{R_2} = 0$$

$$-4m - \frac{v_2}{6k} + \frac{v_1}{6k} - \frac{v_2}{6k} = 0$$

$$\frac{v_1}{6k} - \frac{v_2}{3k} = 4 \times 10^{-3}$$

→ B

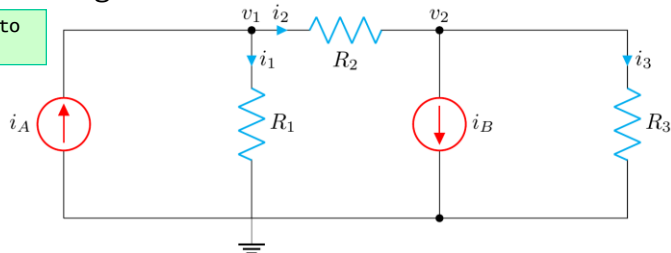Now we have two equations (A,B) and you can use any method that you know to solve the two equations for two unknown voltages. I am using method of substitution on next page



20

20

Multi-node Analysis

- Prob. 2(cont.): Given: $i_A = 1mA$, $R_1 = 12k\Omega$, $R_2 = 6k\Omega$, $i_B = 4mA$ and $R_3 = 6k\Omega$. Determine all node voltages, and currents.

From A, get v_1

$$\frac{v_1}{4k} = \frac{v_2}{6k} + 1 \times 10^{-3}$$

$$v_1 = \frac{2v_2}{3} + 4$$

→ A'

Substitute v_1 in B

$$\frac{1}{6k} \times \left(\frac{2v_2}{3} + 4 \right) - \frac{v_2}{3k} = 4 \times 10^{-3}$$

$$\frac{2v_2}{3} + 4 - 2v_2 = 24$$


$$2v_2 + 12 - 6v_2 = 72$$

$$v_2 = -15V$$

Substitute v_2 in A'

$$v_1 = \frac{2 \times -15}{3} + 4$$

$$v_1 = -6V$$

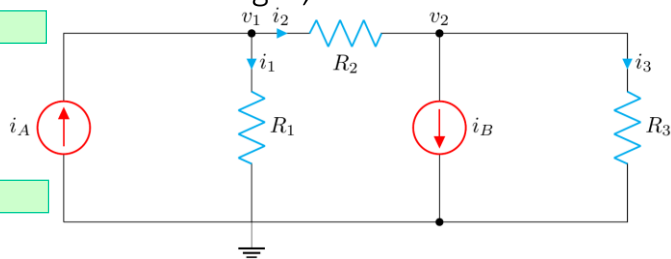

21

21

Multi-node Analysis


- Prob. 2(cont.): Given: $i_A = 1mA$, $R_1 = 12k\Omega$, $R_2 = 6k\Omega$, $i_B = 4mA$ and $R_3 = 6k\Omega$. Determine all node voltages, and currents.

Knowing the node voltages, we can determine all the currents using Ohm's law

$$i_1 = \frac{v_1}{R_1} = -\frac{6}{12k} = -0.5mA$$

$$i_2 = \frac{v_1 - v_2}{R_2} = \frac{-6 + 15}{6k} = \frac{9}{6k} = 1.5mA$$
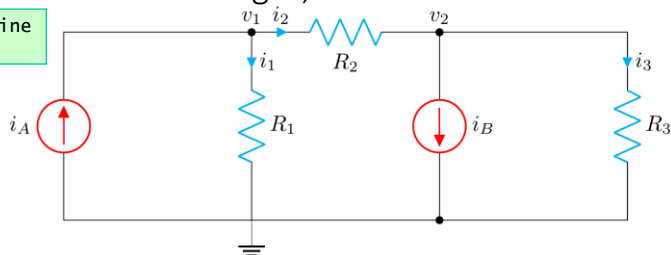
$$i_3 = \frac{v_2}{R_3} = -\frac{15}{6k} = -2.5mA$$



22

22

White Board

23

23