



Full resolution photo on my Instagram [@feenafoto](https://www.instagram.com/feenafoto)

1

ECOR1043: Circuits


Resistive Circuits

Ohm's Law and Kirchhoff's Laws

3

Ohm's Law

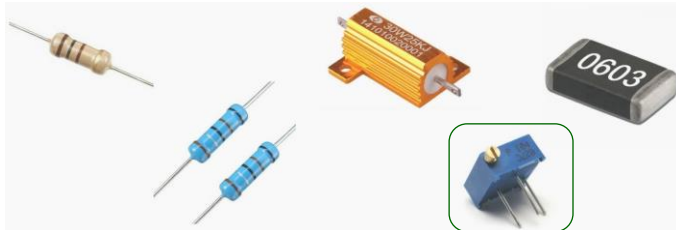- Resistance R
 - The resistance R of an element denotes its ability to resist the flow of electric current
 - Resistance is measured in **ohms Ω**
 - An element with this property is called a **resistor**
 - Resistor could also be variable



Source: All about eelectronics

Ohm's Law and Kirchhoff's Laws

4



4

Ohm's Law

- Ohm's law
 - The voltage across a resistance is directly proportional to the current flowing through it

$$v(t) = i(t)R$$

$$V = IR$$

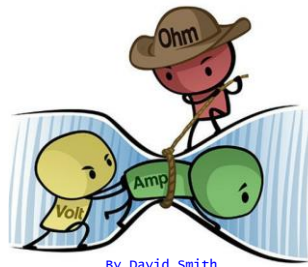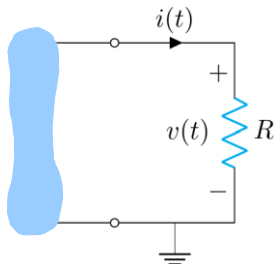

By David Smith


Ohm's Law and Kirchhoff's Laws

5


5

Ohm's Law


- Special Cases of Resistance

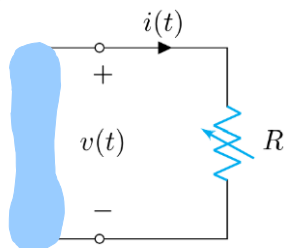

Variable Resistor

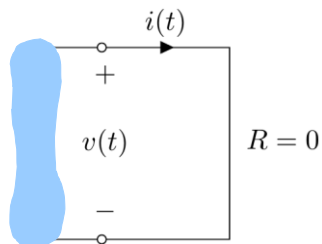

Short-Circuit

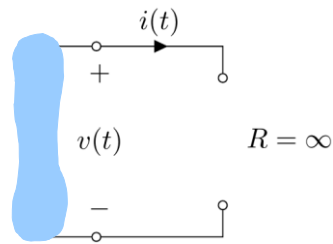

Open-Circuit

- What about the current?

Ohm's Law and Kirchhoff's Laws

6

Ohm's Law

- Typical problems and how to solve them using Ohm's Law

$$v = iR$$


One equation and three variables.
Given ANY two we solve for the third.

- Ex. 1: Given current and resistance, find the **voltage** across the resistor

Hint: Use PSC to determine voltage polarity

$$v = iR$$
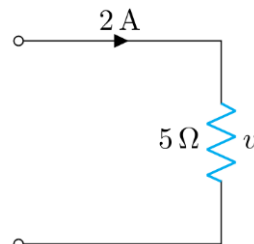
$$v = iR = (2\text{ A})(5\ \Omega) = 10\text{ V}$$




Ohm's Law and Kirchhoff's Laws


7

Ohm's Law

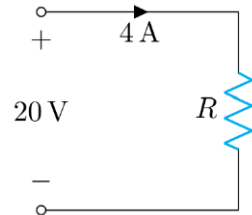- Ex. 2: Given the current and voltage, find the **resistance** of the resistor



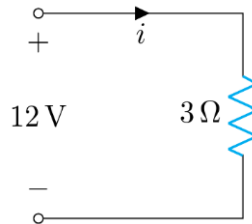- Ex. 3: Given the voltage and resistance, find the **current** through the resistor



$$R = \frac{v}{i} = \frac{20 \text{ V}}{4 \text{ A}} = 5 \Omega$$

$$i = \frac{v}{R} = \frac{12 \text{ V}}{3 \Omega} = 4 \text{ A}$$

Ohm's Law and Kirchhoff's Laws

8

8

Ohm's Law

- Resistors and electric power
 - Combining Ohm's law and the expressions for power we can derive several useful expressions

$$V = IR \longrightarrow \text{A}$$

$$P = VI \longrightarrow \text{B}$$

- Therefore, substituting V from eq. A into eq. B, we get

$$P = I^2 R$$

- And substituting I from eq. A into eq. B, we get

$$P = \frac{V^2}{R}$$

- So, we have three equations to compute power

$$P = VI$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

Ohm's Law and Kirchhoff's Laws

9

9

Ohm's Law

- Ex. 4: Determine the **current** and the **power** associated with the resistor

$$i=?$$

$$v = iR$$

$$v = 12V$$

$$R = 2k\Omega$$

$$i = \frac{v}{R} = \frac{12V}{2k\Omega} = 6mA$$

$$P=?$$


$$P = vi$$

$$P = (12V)(6mA) = 72mW$$

Can you use any other formula to compute P?

$$P = I^2R$$

$$P = \frac{V^2}{R}$$

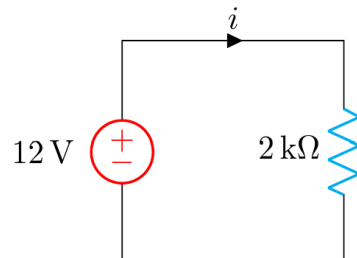

Ohm's Law and Kirchhoff's Laws

10

10

Ohm's Law

- Ex. 5: Find the **resistance** of the lamp and the **current** through the lamp.

$$V = 12V$$

$$P = 60W$$

$$R=?$$

$$P = VI$$

$$P = I^2R$$

$$P = V^2/R$$

$$P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P} = \frac{(12V)^2}{60W} = 2.4\Omega$$

$$I=?$$

$$V = 12V$$

$$P = 60W$$

$$R = 2.4\Omega$$

$$V = IR$$


$$P = VI$$

$$P = I^2R$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{12V}{2.4\Omega} = 5A$$

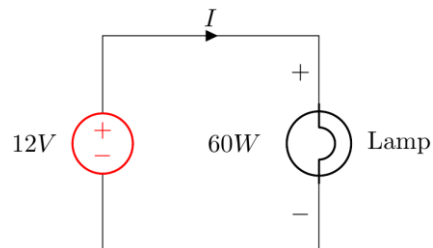Equivalently, we could have used $P=VI$ or $P=I^2R$ to find I




Ohm's Law and Kirchhoff's Laws

11

11

Circuit Concepts and Terms

- Branch b
 - A branch represents a single element such as a voltage source or a resistor. (e.g., component R_4)
- Node n
 - A node is the point of connection between two or more branches (e.g., big node 1)
- Loop l
 - A closed path that never goes twice over a node (e.g., the blue line)
 - The red path is not a loop
 - A loop is said to be *independent* if it contains at least one branch which is not a part of any other independent loop

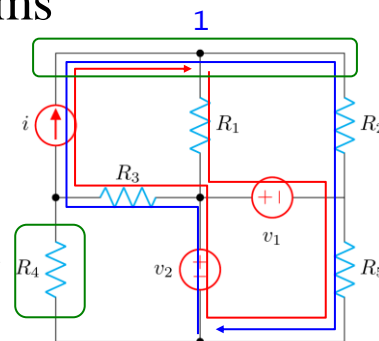

$$l = b - n + 1$$

Where l is the maximum number of independent loops

Ohm's Law and Kirchhoff's Laws


12

12

Circuit Concepts and Terms

- Ex. 6: Determine number of branches (b), number of nodes (n) and maximum number of independent loops (l) for the following circuit:


$$l = b - n + 1$$

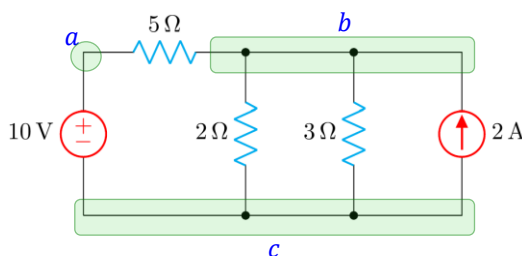

Branches?

$$b = 5$$

$$l = b - n + 1 \\ = 5 - 3 + 1 = 3$$

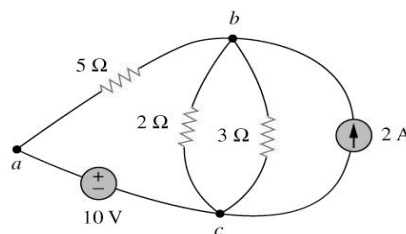

Nodes

$$n = 3$$

Ohm's Law and Kirchhoff's Laws


13

13

Kirchhoff's Current Law (KCL)

- The algebraic sum of the currents entering (or leaving) any node is zero*

$$\sum_{n=1}^N i_n = 0$$

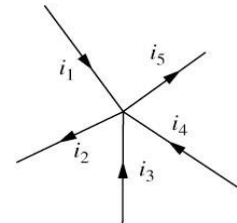

- The sum of the currents entering a node is equal to the sum of the currents leaving the node*
- Kirchhoff's current law is based on the principle of conservation of charge
- We assume signs of the currents and stay consistent*

Ohm's Law and Kirchhoff's Laws

14

14

Kirchhoff's Current Law (KCL)

- Ex 7: Find the missing current i_x


Algebraic sum of currents into Node is zero

Assuming the currents exiting the node are +ve

$$i_x + 4A - (-3A) - 2A = 0$$

$$i_x + 4A + 3A - 2A = 0$$

$$i_x = -5A$$

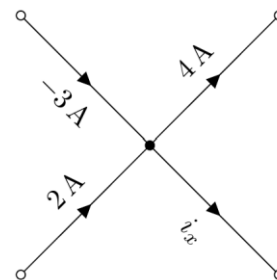

Ohm's Law and Kirchhoff's Laws

15

15

Kirchhoff's Current Law (KCL)

- Ex 8: Find the missing current i


Algebraic sum of currents into Node 1 is zero

Assuming the currents exiting the node are +ve

$$50m + 30m - 5m + i = 0$$

$$75 + i = 0$$

$$i = -75mA$$

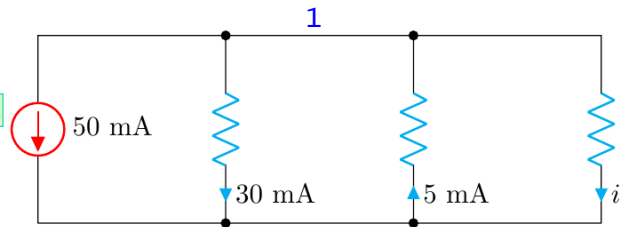

Ohm's Law and Kirchhoff's Laws


16

16

Kirchhoff's Voltage Law (KVL)

- The algebraic sum of the voltages around any loop is zero*

$$\sum_{m=1}^M v_m = 0$$

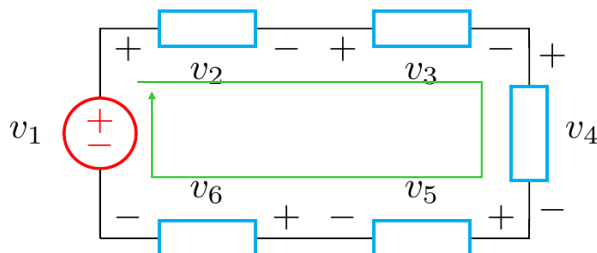

- To apply KVL, we must traverse any loop in the circuit and sum to zero the increases and decreases in energy level
- As we move around a loop, we encounter the plus sign first for a decrease in energy level and a negative sign first for an increase in energy level
- Kirchhoff's voltage law is based on the conservation of energy

Ohm's Law and Kirchhoff's Laws

17

17

Kirchhoff's Voltage Law (KVL)

- Ex. 9: Given V_{R1} and V_{R2} , find V_{R3} using KVL and $P_{2k\Omega}$

$$V_{R1} = 18 \text{ V}$$

$$V_{R2} = 12 \text{ V}$$

For V_{R3}


$$V_{R1} - 5 \text{ V} + V_{R2} - 15 \text{ V} + V_{R3} - 30 \text{ V} = 0$$

$$18 - 5 \text{ V} + 12 - 15 \text{ V} + V_{R3} - 30 \text{ V} = 0$$

$$V_{R3} = 20 \text{ V}$$

For power $P_{2k\Omega}$
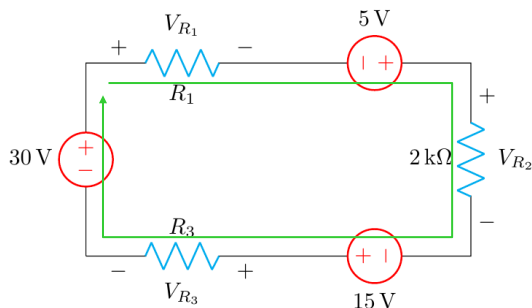
$$P_{2k\Omega} = \frac{V_{R2}^2}{R_2} = \frac{(12)^2}{2k} = 72 \text{ mW}$$



Ohm's Law and Kirchhoff's Laws

18

18

Kirchhoff's Voltage Law (KVL)

- Ex. 10: Find the number of **branches**, **nodes**, **maximum independent loops**, and write the **KVL equations** for all loops.

b?

$$b=7$$

n?

$$n=6$$

l?

$$l = b - n + 1$$

$$l = 7 - 6 + 1 = 2$$


Hence there are only 2 independent KVL equations

$$V_{R1} + V_{R4} - 16 \text{ V} - 24 \text{ V} = 0$$

$$V_{R2} + V_{R3} + 8 \text{ V} + 16 \text{ V} - V_{R4} = 0$$

$$V_{R1} + V_{R2} + V_{R3} + 8 \text{ V} - 24 \text{ V} = 0$$

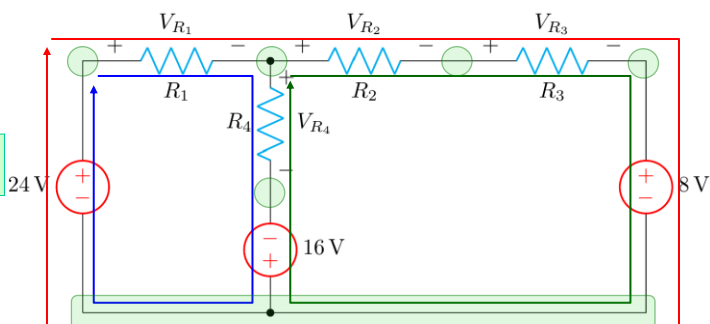The third equation is the sum of the other two!!



Ohm's Law and Kirchhoff's Laws

19

19

Practice Problems


Ohm's Law and Kirchhoff's Laws

20

20

Ohm's Law

- Prob. 1: Determine $i(t)$

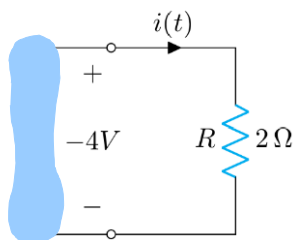


OHM'S LAW

$$v(t) = Ri(t)$$

$$-4[V] = (2\Omega)i(t) \Rightarrow i(t) = -2[A]$$

This problem could be given like this

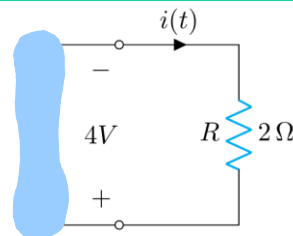

OHM'S LAW

$$v(t) = -Ri(t)$$


Ohm's Law and Kirchhoff's Laws

21

21

Ohm's Law

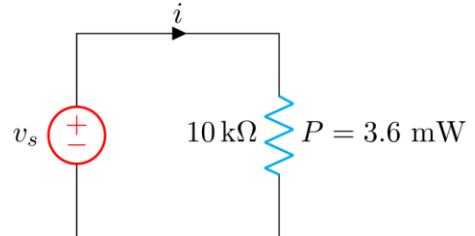- Prob. 2
 - Determine current and voltage



- Ans: $v = 6\text{V}$, $i = 0.6\text{mA}$


Ohm's Law and Kirchhoff's Laws

22

22

Ohm's Law

- Prob. 3
 - Determine R and v_s

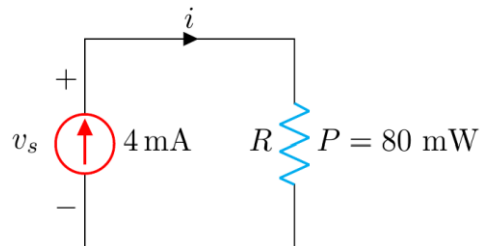

- Ans: $R=5\text{k}\Omega$, $v_s=20\text{V}$

Ohm's Law and Kirchhoff's Laws

23

23

Kirchhoff's Current Law (KCL)


- Prob. 4: Find the missing current i_x

Sum of currents into Node is zero

Assuming the currents entering the node are +ve

$$5\text{ A} + i_x - 3\text{ A} = 0$$

$$i_x = -2\text{ A}$$

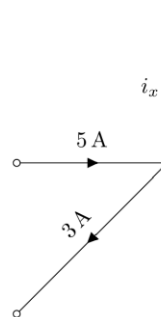

Do the same calculation, assuming current leaving the node are +ve, what happens?


Ohm's Law and Kirchhoff's Laws

24

24

Kirchhoff's Current Law (KCL)

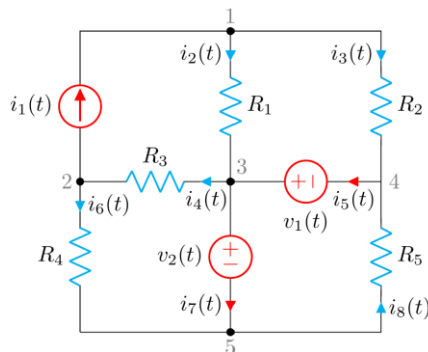- Prob. 5: Write KCL for node 3
 - Assuming currents entering the node are +



$$\text{Ans: } i_2(t) + i_5(t) - i_7(t) - i_4(t) = 0$$

Ohm's Law and Kirchhoff's Laws

25

25

Kirchhoff's Current Law (KCL)

- Prob. 6: Find the missing currents, I_1 , I_4 , I_5 and I_6


Assuming the currents **exiting** the nodes are +ve, write KCL for each node

$$(1) -I_1 + 60 \text{ mA} + 20 \text{ mA} = 0$$

$$(2) I_1 - I_4 + I_6 = 0$$

$$(3) -60 \text{ mA} + I_4 - I_5 + 40 \text{ mA} = 0$$
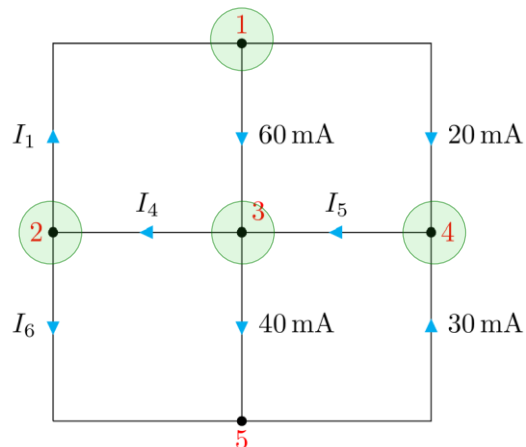
$$(4) -20 \text{ mA} + I_5 - 30 \text{ mA} = 0$$



Ohm's Law and Kirchhoff's Laws

26

26

Kirchhoff's Current Law (KCL)


- Prob. 6 (cont.): Find the missing currents, I_1 , I_4 , I_5 and I_6

For I_1 (1) $-I_1 + 60 \text{ mA} + 20 \text{ mA} = 0$

For I_5 (4) $-20 \text{ mA} + I_5 - 30 \text{ mA} = 0$

For I_4 (3) $-60 \text{ mA} + I_4 - I_5 + 40 \text{ mA} = 0$

For I_6 (2) $I_1 - I_4 + I_6 = 0$

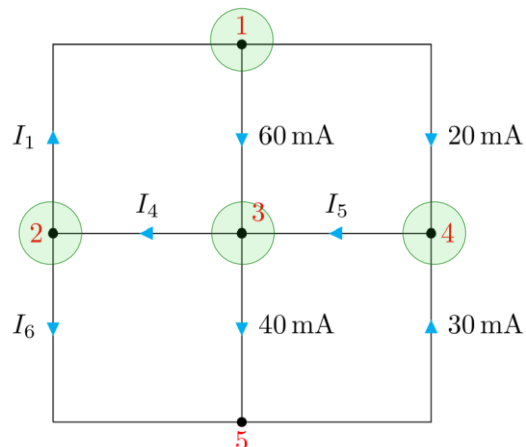

$$I_1 = 80 \text{ mA}$$

$$I_5 = 50 \text{ mA}$$

$$I_4 = 70 \text{ mA}$$

$$I_6 = -10 \text{ mA}$$


Ohm's Law and Kirchhoff's Laws

27


27

Kirchhoff's Current Law (KCL)


- Prob. 7: Find i_1

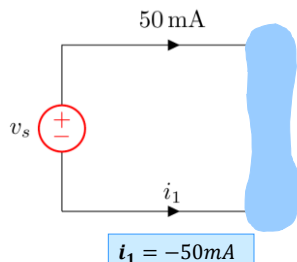


- Prob. 8: Find I_T

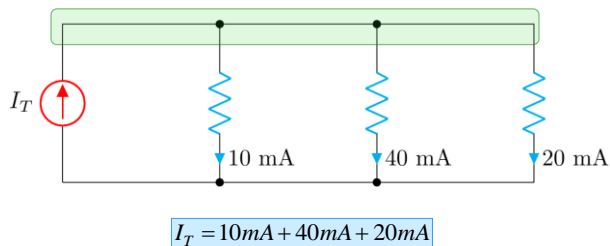

- Prob. 9: Find i_1

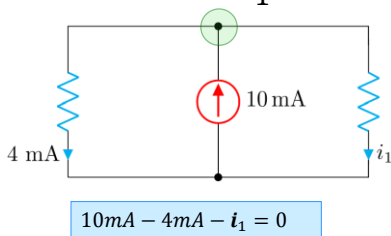

- Prob. 10: Find i_1 and i_2

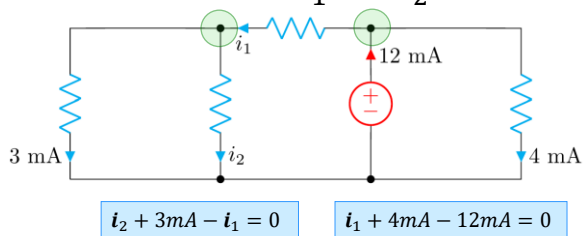

Ohm's Law and Kirchhoff's Laws


28

28

Kirchhoff's Voltage Law (KVL)

- Prob. 11: Write the KVL equation

$$V_{R1} + V_{R2} + V_{R3} - V_S = 0$$

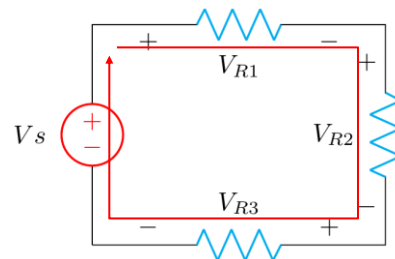

Ohm's Law and Kirchhoff's Laws

29

29

Kirchhoff's Voltage Law (KVL)

- Prob. 12: Given V_2 , find V_x , and $P_{2k\Omega}$


We need to find a closed path where only one voltage is unknown

To find V_x $V_2 = 4\text{ V}$

$$V_x + V_3 - V_1 + V_2 = 0$$

$$V_x + 4\text{ V} - 12\text{ V} + 4\text{ V} = 0$$

$$V_x = 4\text{ V}$$

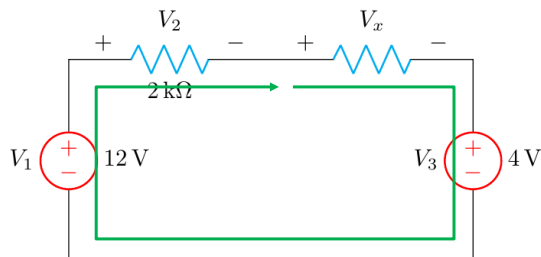

Ohm's Law and Kirchhoff's Laws

30

30

Kirchhoff's Voltage Law (KVL)

- Prob. 12 (cont.): Given V_2 , find V_x , and $P_{2k\Omega}$

To find $P_{2k\Omega}$ $V_2 = 4\text{ V}$

$$P_{2k\Omega} = \frac{V_2^2}{R_2}$$

$$P_{2k\Omega} = \frac{(4\text{ V})^2}{2\text{ k}\Omega}$$

$$P_{2k\Omega} = 8\text{ mW}$$

$$V_2 = 4\text{ V}$$

Ohm's Law and Kirchhoff's Laws

31

31

White Board

Ohm's Law and Kirchhoff's Laws

32