



Full resolution photo on my Instagram [@feenafoto](#)

1

ECOR1043: Circuits

Multi-loop Analysis


Develop systematic techniques to determine all the currents in a circuit

3

3

Multi-Loop Analysis

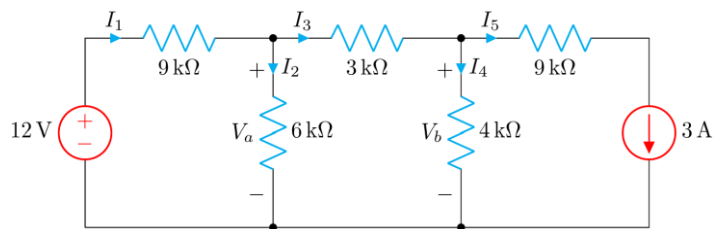- A Multi-Loop circuit is a circuit with more loops than the basic one loop circuit we discussed
 - Due to the added loops, analysis becomes more complex
 - Therefore, we introduce a new type of analysis
- Multi-Loop Analysis: Mesh Analysis
 - This method uses the “Loop” equations of [Kirchhoff's Voltage Law](#) as well as [Ohm's Law](#) to find the various [currents](#) around the circuit.




4

4

Nodal or Loop Analysis?

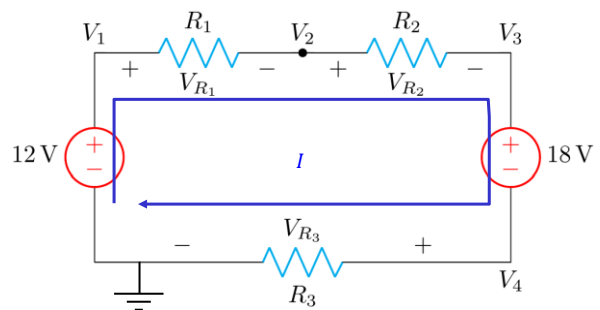- What if we try to apply nodal analysis to this circuit?
 - There are 4 non-reference nodes
 - There is one node connected to the reference through a voltage source
 - We know that $V_1 = 12V$, so we need three equations to compute all node voltages
 - But there is [only one current](#) flowing through all components and if that current is determined all voltages can be computed with ohm's law



When a voltage source is connected to two non-reference nodes, nodal analysis is more involved

When a current source shared by two meshes, mesh analysis is more involved


- So, we base our analysis on KVL instead

5

5

Definitions and Terms

- Definitions:
 - **Loop**: A closed path that does not go over any node twice
 - This circuit has three loops (red, blue, green)
 - **Mesh**: A loop that does not enclose any other loop. [fabef] and [ebcde] are meshes.
 - **Loop Current**: A (fictitious) current that is assumed to flow around a loop. I_1 , I_2 , and I_3 are loop currents.
 - **Mesh Current**: A loop current associated with a mesh. I_1 , I_2 are mesh currents, I_3 is not
 - We can calculate currents through various component by using loop currents

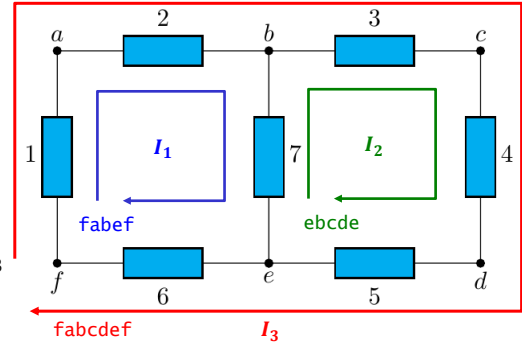

6

Multi-Loop Analysis

- In a circuit, the current through any component can be expressed in terms of the loop (fictitious) currents.
- Ex. 1: Express the currents I_{af} , I_{be} , and I_{bc} in terms of I_1 , I_2 , and I_3

$$I_{af}$$


$$I_{af} = -I_1 - I_3$$

$$I_{be}$$

$$I_{be} = I_1 - I_2$$

$$I_{bc}$$

$$I_{bc} = I_2 + I_3$$

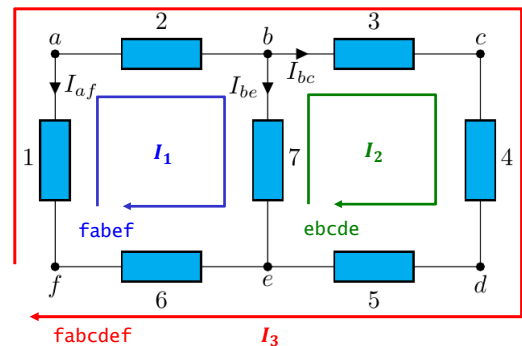

7

Multi-Loop Analysis

- Just because a loop exists does not mean it is independent
 - In last slide, one of the loops is dependent
- Ex. 2: Express the currents I_{af} , I_{be} , and I_{bc} in terms of I_1 and I_3 only

I_{af}


$$I_{af} = -I_1 - I_3$$

I_{be}

$$I_{be} = I_1$$

I_{bc}

$$I_{bc} = I_3$$

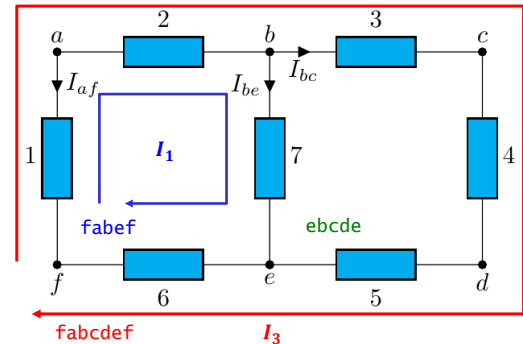

For every circuit there is a minimum number of loop currents that are necessary to compute every current in the circuit.


This is equal to the number of independent loops in that circuit:
 $(l = b - n + 1)$

8

8

Multi-Loop Analysis

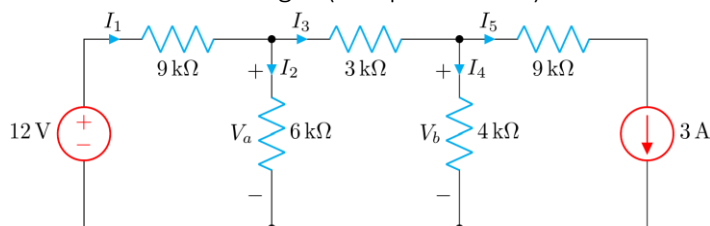- Steps for Mesh Analysis:
 - Determine how many mesh/loops do we need
 - Identify all mesh's and assign mesh currents
 - Identify all known currents
 - For each loop with an unknown current, write a KVL equation
 - Replace voltages in terms of mesh currents
 - Solve for mesh currents
 - Solve for unknown currents as needed
 - Use currents to solve for voltages (and powers etc.)



9

9

Multi-Loop Analysis

- Ex. 3: Find the equations that can be used to solve for element currents i_a , i_b and i_c

0. Let's see how many independent loop/mesh we need.

$$\begin{aligned} B &= 7 \\ N &= 6 \\ L &= B - (N - 1) \\ &= 7 - (6 - 1) = 2 \end{aligned}$$

1. Identify all mesh's and assign mesh currents

2. Identify all known currents

There is none ☹

3. For each loop with an unknown current, write a KVL equation

KVL on left mesh (Loop 1)

$$v_1 + v_3 + v_2 - v_{s1} = 0$$

KVL on right mesh (Loop 2)

$$v_{s2} + v_4 + v_5 + v'_3 = 0$$

You may skip this step and directly go to next step

4. Replace voltages in terms of mesh currents


$$i_1 R_1 + (i_1 - i_2) R_3 + i_1 R_2 - v_{s1} = 0$$

$$v_{s2} + i_2 R_4 + i_2 R_5 + (i_2 - i_1) R_3 = 0$$

$$i_1 R_1 + i_1 R_3 - i_2 R_3 + i_1 R_2 - v_{s1} = 0$$

$$v_{s2} + i_2 R_4 + i_2 R_5 + i_2 R_3 - i_1 R_3 = 0$$

10

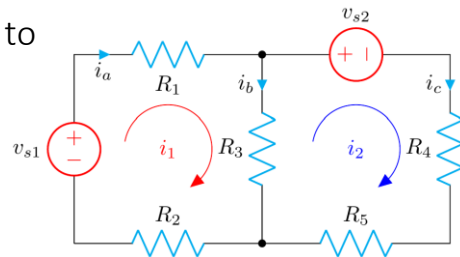

10

Multi-Loop Analysis

- Ex. 3(cont.): Find the equations that can be used to solve for element currents i_a , i_b and i_c

$$i_1(R_1 + R_2 + R_3) - i_2 R_3 = v_{s1}$$

$$-i_1 R_3 + i_2(R_3 + R_4 + R_5) = -v_{s2}$$

Two unknowns (i_1, i_2) and two equations, which we can solve using various methods

Step (cont.):

5. Solve for mesh currents

$$i_1, i_2$$


6. Solve for unknown currents as needed

Once mesh currents i_1 and i_2 are known, we can find the desired currents

$$i_a = i_1, i_b = i_1 - i_2 \text{ and } i_c = i_2$$

7. Use currents to solve for voltage (and powers)

There is even a more direct way ☺

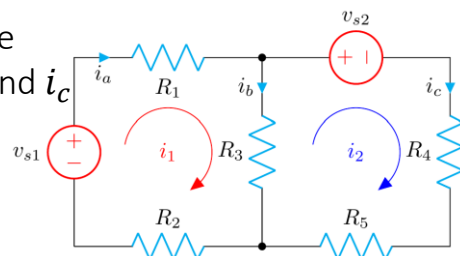

11

11

Multi-Loop Analysis

• Ex 4: Find I_o

1. First, assign mesh current I_1 and I_2

2. Identify all known currents There is none ☹


3. For each loop with an unknown current, write a KVL directly replacing voltages in terms of mesh currents

1) KVL for loop 1:

$$-12V + 6k\Omega(I_1) + 6k\Omega(I_1 - I_2) = 0 \quad \text{Loop 1}$$

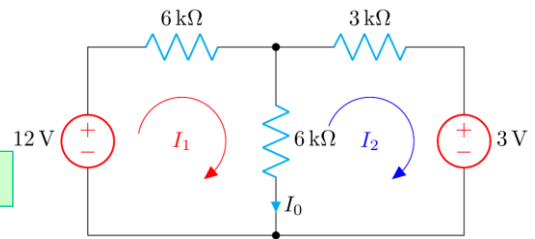2) KVL for loop 2:

$$6k\Omega(I_2 - I_1) + 3k\Omega(I_2) + 3V = 0 \quad \text{Loop 2}$$



12

12

Multi-Loop Analysis

• Ex. 4 (cont.): Find I_o

Simplify KVL for loop 1

$$-12V + 6k\Omega(I_1) + 6k\Omega(I_1 - I_2) = 0$$

$$-12V + 6k\Omega(I_1) + 6k\Omega I_1 - 6k\Omega I_2 = 0$$


$$12k\Omega I_1 - 6k\Omega I_2 = 12V \quad \text{A}$$

Simplify KVL for loop 2

$$6k\Omega(I_2 - I_1) + 3k\Omega(I_2) + 3V = 0$$

$$6k\Omega I_2 - 6k\Omega I_1 + 3k\Omega(I_2) + 3V = 0$$
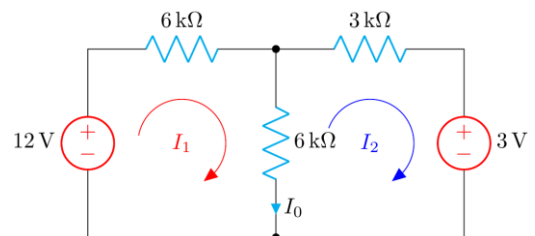
$$-6k\Omega I_1 + 9k\Omega I_2 = -3V \quad \text{B}$$



Let's try them in a more direct way

13

13

Multi-Loop Analysis

- Ex. 4 (cont.): Find I_0

$$(12k\Omega)I_1 - (6k\Omega)I_2 = 12V \quad A$$

$$(-6k\Omega)I_1 + (9k\Omega)I_2 = -3V \quad B$$

Multiply eq. B with 2 and add A and B

$$(12k\Omega)I_1 - (6k\Omega)I_2 = 12V \quad A$$

$$(-12k\Omega)I_1 + (18k\Omega)I_2 = -6V \quad B'$$

$$12kI_2 = 6V$$

$$I_2 = 0.5mA$$

Substitute I_2 back in B

$$(-6k\Omega)I_1 + (9k\Omega) \times 0.5m = -3V$$


$$(-6k\Omega)I_1 = -3V - 4.5V$$

$$I_1 = \frac{-3V - 4.5V}{(-6k\Omega)}$$

$$I_1 = 1.25mA$$

5. Solve for mesh currents (by using process of Elimination)

Add A and B'

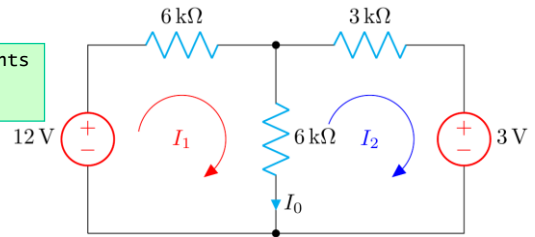

So, mesh currents are

$$I_1 = 1.25mA$$

$$I_2 = 0.5mA$$

6. Solve for unknown currents as needed

We know I_1 and I_2 but we want to find I_0

$$I_0 = I_1 - I_2$$

$$I_0 = 1.25mA - 0.5mA$$

$$I_0 = 0.75mA$$

14

14

Multi-Loop Analysis

- Ex.5: Find both v_o and v_2

For v_o

1. First, assign mesh current I_1 and I_2

2. Identify all known currents

Current sources that are not shared by other meshes (or loops) serve to define a mesh (loop) current and reduce the number of required equations

Mesh 1 eq

Mesh 1 current is constrained

$$I_1 = 2mA$$

Mesh 2 equation

$$6kI_2 + 2k(I_2 - I_1) - 2 = 0$$

$$6kI_2 + 2kI_2 - 2kI_1 - 2 = 0$$

$$8kI_2 - 2kI_1 = 2$$

Substitute I_1

$$8kI_2 - 2k \times 2m = 2$$

$$8kI_2 - 4 = 2$$

$$8kI_2 = 6$$

$$I_2 = \frac{6}{8k} = 0.75mA$$

Now we can find v_o

$$v_o = 6k \times I_2 = 6k \times 0.75m = 4.5V$$

Now we will find v_2

$$v_2 = (I_1 - I_2) \times 2k$$


$$v_2 = (2m - 0.75m) \times 2k$$

$$v_2 = 1.25m \times 2k$$

$$v_2 = 2.5V$$

15

15

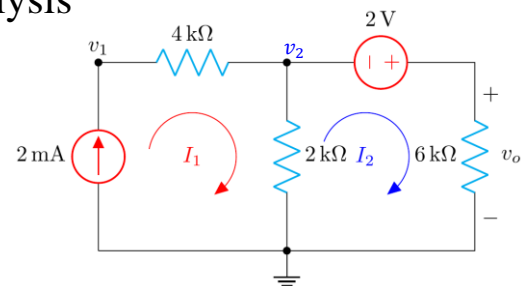

Practice Problems

16

16

Multi-Loop Analysis

- Prob 1: Ex. 4 Alternative Solution: Find I_o

Earlier (ex.4) we used mesh currents as shown in top right figure

Alternatively, we can use different mesh/loop currents as shown in bottom right figure and get same answer

KVL @ I_1 $-12 + 6k(I_1 + I_2) + 6kI_1 = 0$ A

KVL @ I_2 $-12 + 6k(I_1 + I_2) + 3kI_2 + 3 = 0$ B

NOW $I_o = I_1$

This selection is better as we can find I_o directly

Rearrange

$12kI_1 + 6kI_2 = 12$ A'

$6kI_1 + 9kI_2 = 9$ B'

Use Process of Elimination to solve
Multiply B' by 2 and subtract from A',


$-12kI_2 = -6 \Rightarrow I_2 = 0.5mA$

$I_1 = \frac{9 - 9k \times 0.5mA}{6k} \Rightarrow I_1 = 0.75mA$

Therefore

$I_o = I_1 = 0.75mA$

which is what we got before.

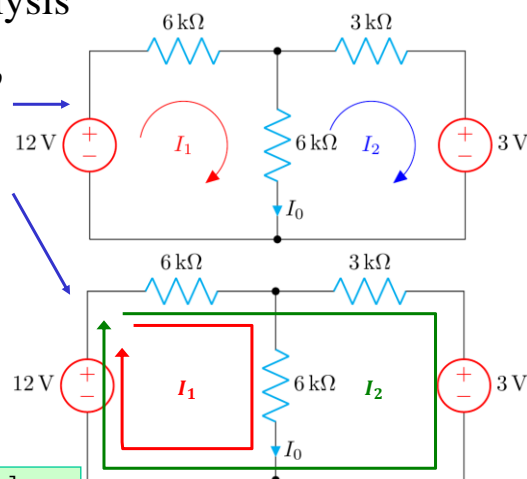

17

Multi-Loop Analysis

- Prob 2: Use mesh equations to find v_o

1. DRAW THE MESH CURRENTS

2. WRITE MESH EQUATIONS

MESH 1

$$(2k + 4k + 2k)I_1 - 2kI_2 = -3[V]$$

$$8kI_1 - 2kI_2 = -3$$

$$8I_1 - 2I_2 = -3m \quad \text{A}$$

MESH 2

$$-2kI_1 + (2k + 6k)I_2 = (6V + 3V)$$

$$-2kI_1 + 8kI_2 = 9$$

$$-2I_1 + 8I_2 = 9m \quad \text{B}$$


Multiply B by 4 and add to A

$$30I_2 = 33m$$

$$I_2 = \frac{33}{30}mA$$

Once I_2 is known we can find v_o

$$v = 6k \times I_2 = \frac{33}{5}V$$

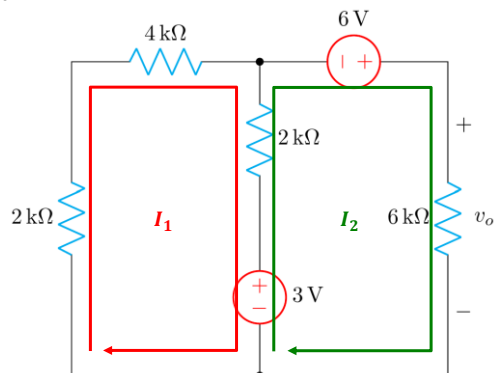

18

18

Multi-Loop Analysis

- Prob 3: Using multi-loop method, find v_o

MESH 1:

$$I_1 = 4mA$$

We actually need the current on the right mesh. Hence, use mesh analysis.

MESH 2:

$$4k(I_2 - I_1) + 6kI_2 + 5 = 0$$

$$10kI_2 - 4kI_1 = -5$$


$$I_2 = \frac{-5 + 4k \times 4m}{10k}$$

$$I_2 = \frac{11}{10}mA$$

After we know I_2 we can find out V_o

$$V_o = 6kI_2 = 6k \times \frac{11}{10}m$$

$$V_o = 6.6V$$

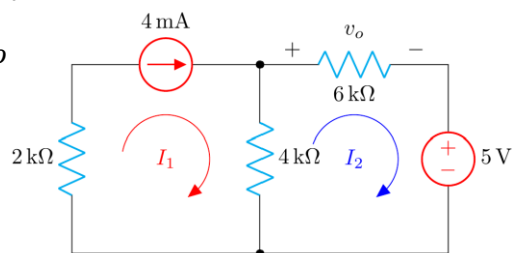

19

19

Multi-Loop Analysis

- Prob 4: In the circuit of Ex.5, find v_1 :

For v_1

v_1 is basically the voltage between point a to reference ground (as there is no second subscript so we assume it to be ground)

To obtain v_1 , apply KVL to any closed path that includes v_1 . We choose green loop path, therefore

$$v_1 + 2k(I_2 - I_1) + 4k \times (-I_1) = 0$$

$$I_1 = 2mA$$


$$I_2 = 0.75mA$$

$$v_1 + 2k(I_2 - I_1) + 4k \times (-2m) = 0$$

$$v_1 + 2k(0.75m - 2m) - 8 = 0$$

$$v_1 - 2.5 - 8 = 0$$

$$v_1 = 10.5V$$

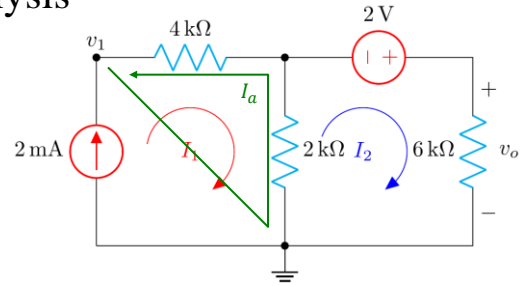

20

Multi-Loop Analysis

- Prob. 5: Ex. 4 Find I_o (Alternate method to solve two equations)

$$(12k\Omega)I_1 - (6k\Omega)I_2 = 12V$$

$$(-6k\Omega)I_1 + (9k\Omega)I_2 = -3V$$

From A, isolate I_1

$$I_1 = \frac{12V + (6k\Omega)I_2}{(12k\Omega)}$$

Substitute in B

$$(-6k\Omega) \times \frac{12V + (6k\Omega)I_2}{(12k\Omega)} + (9k\Omega)I_2 = -3V$$

$$\frac{-12V - (6k\Omega)I_2}{(2k\Omega)} + (9k\Omega)I_2 = -3V$$

$$-12V - (6k\Omega)I_2 + (18k\Omega)I_2 = -6V$$


$$(12k\Omega)I_2 = -6V + 12V$$

$$I_2 = \frac{6V}{12k\Omega}$$

$$I_2 = 0.5mA$$

A Solve them by process of Substitution (instead of Elimination as done before in Ex. 4)

A'

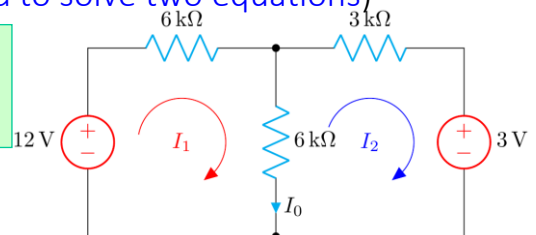

Substitute I_2 in A' and solve for I_1

$$I_1 = \frac{12V + (6k\Omega)I_2}{(12k\Omega)}$$

$$I_1 = 1.25mA$$

We know I_1 and I_2 but we want to find I_o

$$I_o = I_1 - I_2$$

$$I_o = 1.25mA - 0.5mA$$

$$I_o = 0.75mA$$

21

20

21

White Board