



 Full resolution photo on my Instagram [@feenafoto](#)

1


ECOR1043: Circuits

Basics of Frequency Response & Filters

Transfer functions, logarithm, decibels, Bode plots, filters

3


Time and Frequency Domains

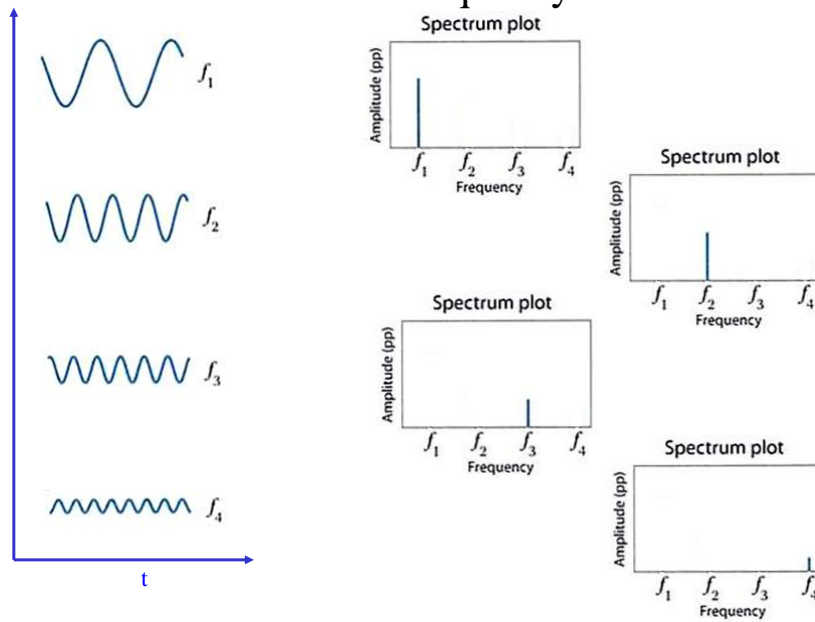

4

4

Time and Frequency Domains

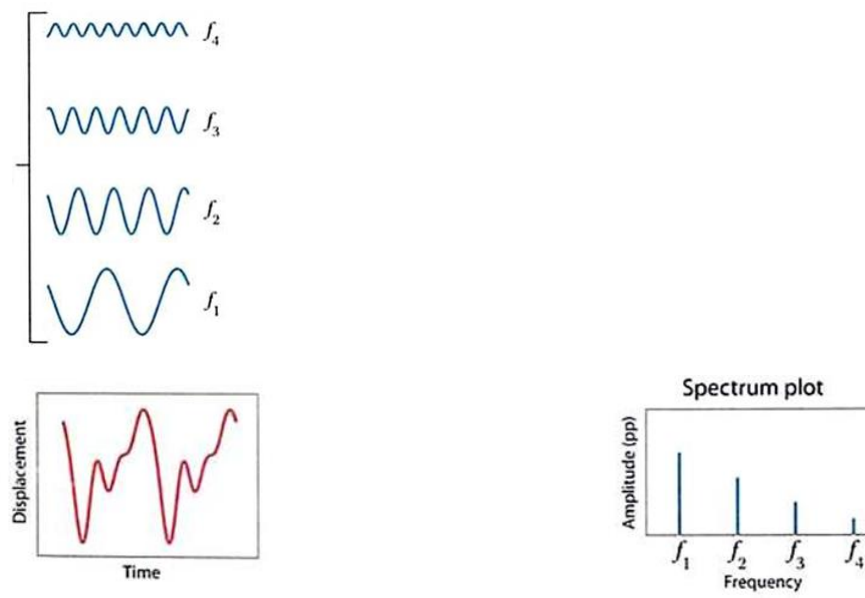

5

5

The Logarithm

- In mathematics, the logarithm is the inverse function to exponentiation.

Base 10 Exp: $10^2 = ? \Rightarrow 100$ Exponent 2

Log: $10^? = 100 \Rightarrow 2$

- The log of a given number x is the exponent to which another number, the base b , must be raised, to produce x . It is denoted by: $\log_b(x)$


- Example 1: What is the logarithm of 1000 in base 10?

$$10^x = 1000 \Rightarrow x = 3$$

Mathematically speaking

$$\log_{10}(1000) = 3$$

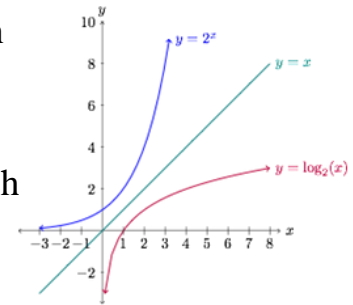In other words, logarithms answers the question:
How many of one number ("base") do we multiply to get another number?



6

6

The Logarithm

- Example 2:
 - What is the logarithm of 16, with a base of 2?

$$\log_2(16) = 4$$

- What is the logarithm of 0.1, with a base of 10?


$$\log_{10}(0.1) = -1$$

7

7

Frequency Response and Transfer Functions

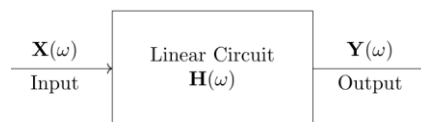- **Frequency response** – the variation in a circuit's behavior with change in signal frequency
- **Transfer function $H(\omega)$** - A frequency dependents ratio of output (response) to the input (source) of a circuit




$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

- Typically given as a ratio of voltages for our applications, comparing output voltage to input voltage

$$H(\omega) = \frac{V_o(\omega)}{V_s(\omega)}$$

$$H = \frac{V_o}{V_s}$$

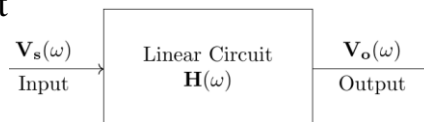

8

8

Transfer Functions - Concept

- Example 3: Find the transfer function ($H=V_o/V_s$) of the circuit below


1) Find V_o in terms of V_s

$$V_o = V_s \left(\frac{10\Omega}{5\Omega + 10\Omega} \right)$$

Using Voltage Divider

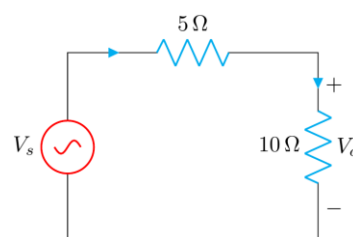2) Solve for $\frac{V_o}{V_s}$

$$H = \frac{V_o}{V_s} = \left(\frac{10\Omega}{5\Omega + 10\Omega} \right) = \frac{2}{3}$$



9

9

Transfer Functions

- Example 4: Find the transfer function ($H=V_o/V_s$) of the circuit below

1) Find V_o in terms of V_s

You can also use voltage divider

$$\frac{V_s - V_o}{5\ \Omega} - \frac{V_o}{10\ \Omega} - \frac{V_o}{5\ \Omega} = 0$$

Using Nodal Analysis


2) Multiply both sides by 10 and rearrange to isolate V_o and V_s

$$\left(\frac{V_s - V_o}{5\ \Omega} - \frac{V_o}{10\ \Omega} - \frac{V_o}{5\ \Omega} \right) \times 10 = 0 \times 10$$

$$2V_s - 2V_o - V_o - 2V_o = 0$$

$$2V_s - 5V_o = 0$$

$$2V_s = 5V_o$$

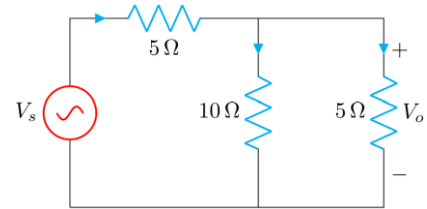

10

10

Transfer Functions

- Example 4(cont.): Find the transfer function ($H=V_o/V_s$) of the circuit below

3) Find $H = \frac{V_o}{V_s}$


$$2V_s = 5V_o$$

$$\frac{V_o}{V_s} = \frac{2}{5}$$

$$\frac{V_o}{V_s} = 0.4$$

$$H = \frac{V_o}{V_s} = 0.4$$

$$H = 0.4$$

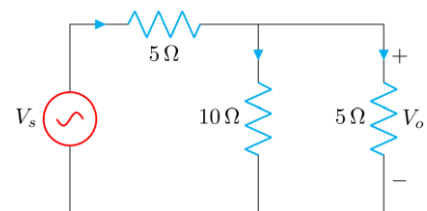


11

11

Linear versus Decibel

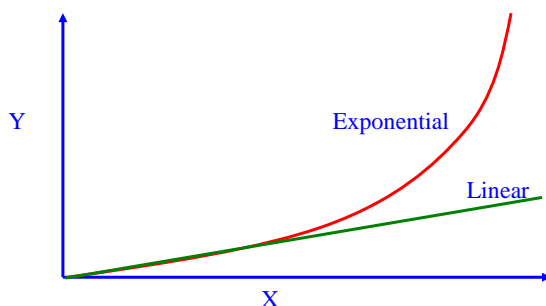- So far, we've calculated voltage in Volts and compared them that way, this is useful for comparing linear relationships, but what if we want to compare something non-linear or exponential?
- While a linear relationship can be plotted relatively easily, the exponential quickly becomes too large to reasonably plot for any large value of x



12

12

Linear versus Decibel

- To account for non-linear relationship, we introduce the units of dB
- The dB is a logarithmic way of describing a ratio. The ratio may be sound pressure, intensity, power, **voltage**, or other quantities
- If we're given a ratio of voltages e.g., output voltage/input voltage:

$$H = \frac{V_0}{V_s}$$

- We can calculate the equivalent in dB using the equation below:

$$\left(\frac{V_0}{V_s}\right)_{dB} = 20\log_{10}\left(\frac{V_0}{V_s}\right)$$

13

13

Calculating Decibels

- Example 5:

a) What is the value of $\frac{V_o}{V_s} = 1$ in dB?

$$\left(\frac{V_o}{V_s}\right)_{dB} = 20\log_{10}\left(\frac{V_o}{V_s}\right)$$

$$20\log_{10}(1) = 0 \text{ dB}$$

b) What is the value of $\frac{V_o}{V_s} = 1000$ in dB?

$$20\log_{10}(1000) = 60 \text{ dB}$$

14

14

Bode Plots - Plotting In Decibels

- Once we have our values in dBs, we can plot our transfer function, this is called a **Bode plot**.
- Bode plot uses **logarithmic axis for frequency and decibels for magnitude**. This permits wider range of frequencies and magnitudes
- Let's generate Bode plot of the transfer function: $H = \frac{V_o}{V_s} = \omega^2$

Frequency (rad/s)	Amplitude [V/V]	Amplitude [dB] = $20\log_{10}(V/V)$
1	1	0
10	100	40
100	10000	80
1000	1000000	120

15


15

Plotting In Decibels

Frequency (rad/s)	Amplitude [V/V]	Amplitude [dB]= 20log ₁₀ (V/V)
1	1	0
10	100	40
100	10000	80
1000	1000000	120

Just the usual plot

$$\frac{V_0}{V_s} = \omega^2$$

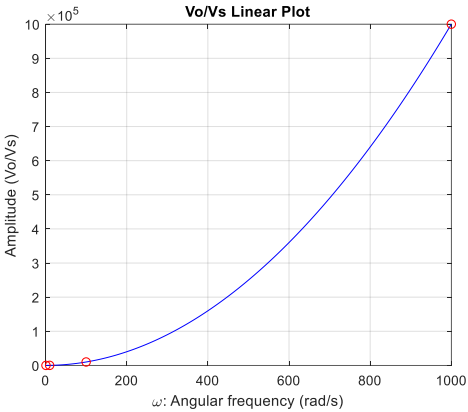


16

16


Plotting In Decibels

Frequency (rad/s)	Amplitude [V/V]	Amplitude [dB]= 20log ₁₀ (V/V)
1	1	0
10	100	40
100	10000	80
1000	1000000	120

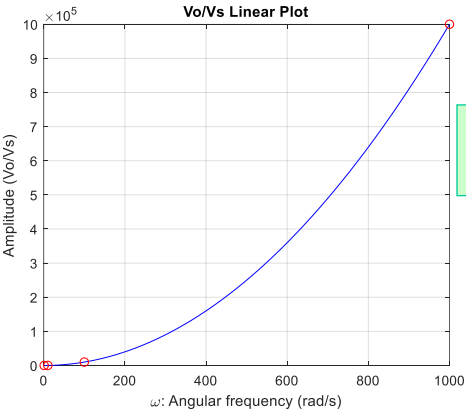

$$H = \frac{V_0}{V_s} = \omega^2$$

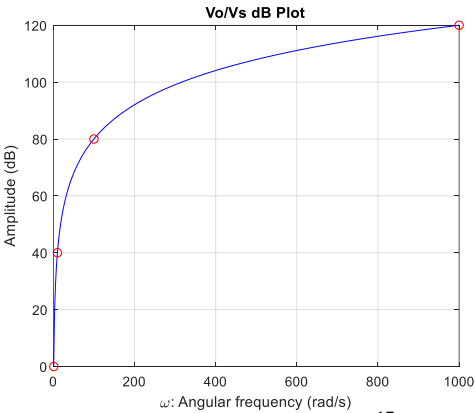Instead of the linear $\frac{V_0}{V_s}$ we plot the y – axis in dB




17

17

Bode Plot - Plotting In Decibels

Frequency (rad/s)	Amplitude [V/V]	Amplitude [dB]= $20\log_{10}(V/V)$
1	1	0
10	100	40
100	10000	80
1000	1000000	120

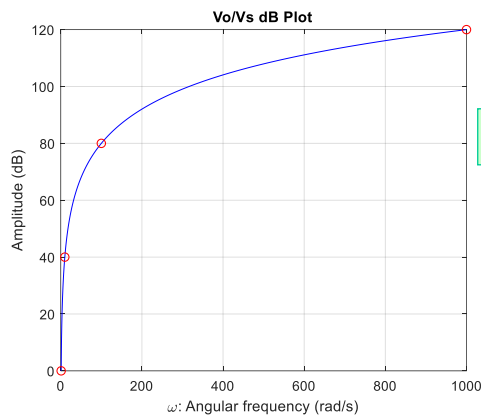


$$H = \frac{V_0}{V_s} = \omega^2$$

Now we change the x axis
to a 'log' scale as well



So what is a 'log' scale?

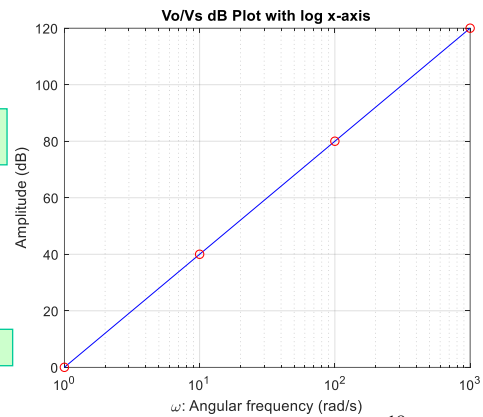

18

18

Bode Plot Example

- Example 6: Create a bode plot for the following transfer function.
Use $\omega = 1, 10, 30, 100, 1000$

$$H = \frac{V_0}{V_s} = \frac{1}{\omega^3}$$

1) First we determine the Amplitude

Frequency (rad/s)	Amplitude [V/V]	Amplitude [dB]= $20\log_{10}(V/V)$
1		
10		
30		
100		
1000		

19

19

Bode Plot Example

- Example 6: Create a bode plot for the following transfer function.
Use $\omega = 1, 10, 30, 100, 1000$

$$H = \frac{V_0}{V_s} = \frac{1}{\omega^3}$$

2) Next we convert it to dB

Frequency (rad/s)	Amplitude [V/V]	Amplitude [dB]= $20\log_{10}(V/V)$
1	1	
10	0.001	
30	0.000037	
100	0.000001	
1000	0.000000001	

20

20

Bode Plot Example

- Example 6: Create a bode plot for the following transfer function.
Use $\omega = 1, 10, 30, 100, 1000$

$$H = \frac{V_0}{V_s} = \frac{1}{\omega^3}$$

$$\left(\frac{V_0}{V_s}\right)_{dB} = 20\log_{10}\left(\frac{V_0}{V_s}\right)$$

3) Now we have our final values, we can plot them


Frequency (rad/s)	Amplitude [V/V]	Amplitude [dB]= $20\log_{10}(V/V)$
1	1	0
10	0.001	-60
30	0.000037	-88.63
100	0.000001	-120
1000	0.000000001	-180

21

21

Bode Plot Example

Frequency (rad/s)	Amplitude [V/V]	Amplitude [dB]= $20\log_{10}(V/V)$
1	1	0
10	0.001	-60
30	0.000037	-88.63
100	0.000001	-120
1000	0.000000001	-180

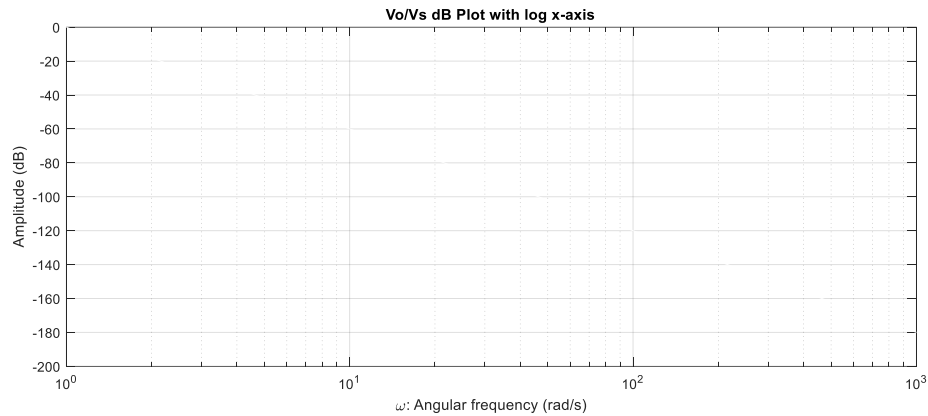


22

22

Bode Plot Example

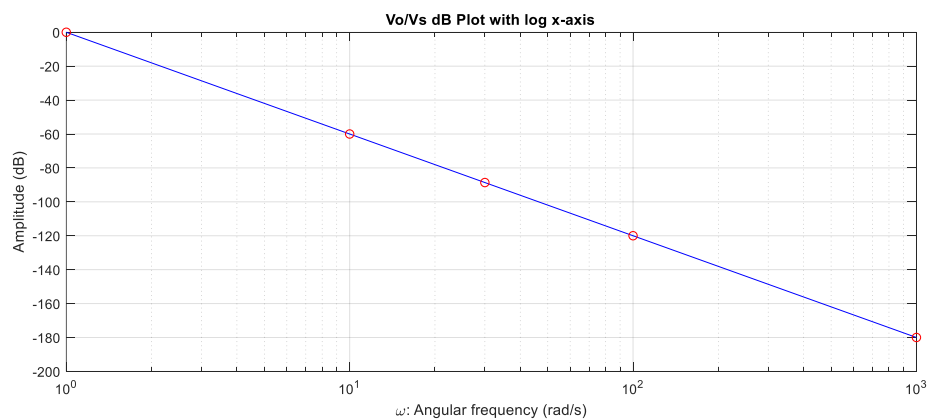- Example 6: Create a bode plot for the following transfer function.
Use $\omega = 1, 10, 30, 100, 1000$

$$H = \frac{V_0}{V_s} = \frac{1}{\omega^3}$$




23

23

Filters

- Filter

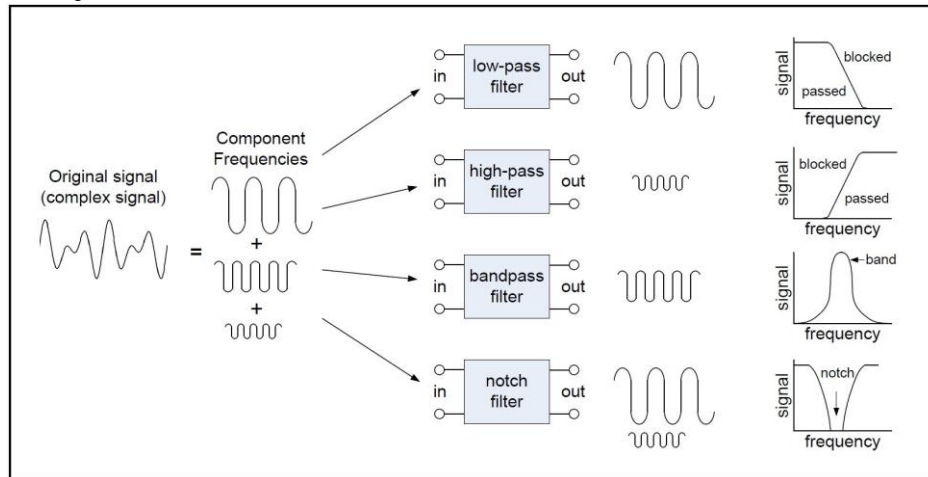- A filter is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others.



<https://www.allaboutcircuits.com/technical-articles/an-introduction-to-filters/>

24

24

Filters

- Categories of filters


- A **passive filter** is one that contains only R, L, and C components.
 - It is not necessary that all three be present. L is often omitted (on purpose) from passive filter design because of the size and cost of inductors etc.
- An **active filter** is one that, along with R, L, and C components, **also contains an energy source**, such as that derived from an operational amplifiers or transistors

25

25

Filters

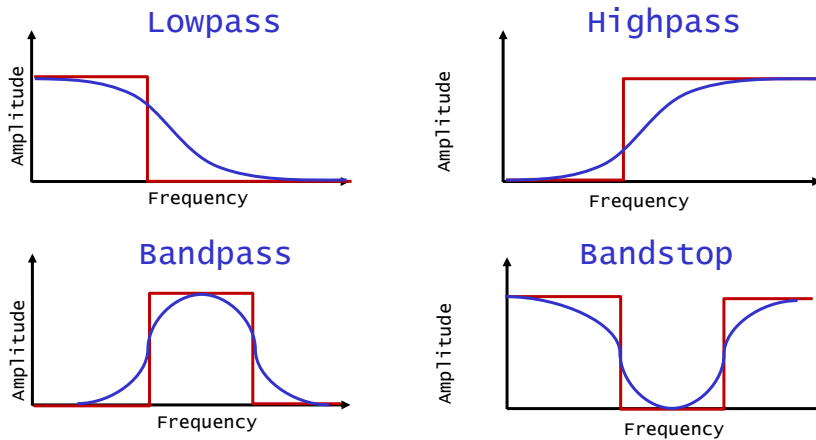- Types of filters
 - Ideal (red) vs. realistic (blue) responses




26


26

Types of filters

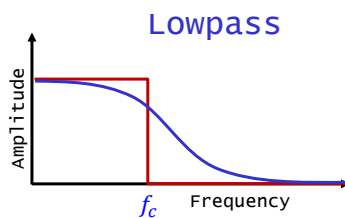- Low-pass Filters
 - Passes frequencies from DC (0 Hz) to f_c and significantly attenuates all others



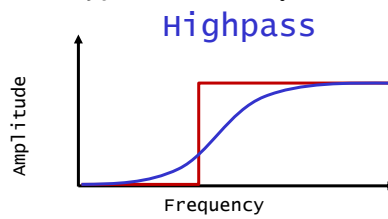- High-pass of filters
 - Passes frequencies from f_c to ∞ (ideally) and significantly attenuates all others




27

27

Bode plots-Filters

- Useful terms

- **Transfer function:** ratio of output (response) to the input (source) of a circuit
- **Passband:** the range of frequencies that are allowed to pass through the filter with minimum attenuation (usually defined as less than -3dB (70.7%) of attenuation)
- **Stopband:** frequencies not in a circuit's passband are in its stopband
- **cutoff frequency f_c :** (also called the critical frequency) separates passband and stopband
- **Bandwidth (BW):** width of the passband
- **Roll-off :** rate at which attenuation increases/decreases after/before the cut-off frequency

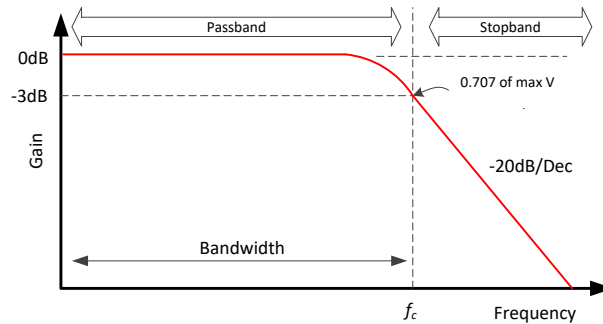

28

28

Thank You

29

29